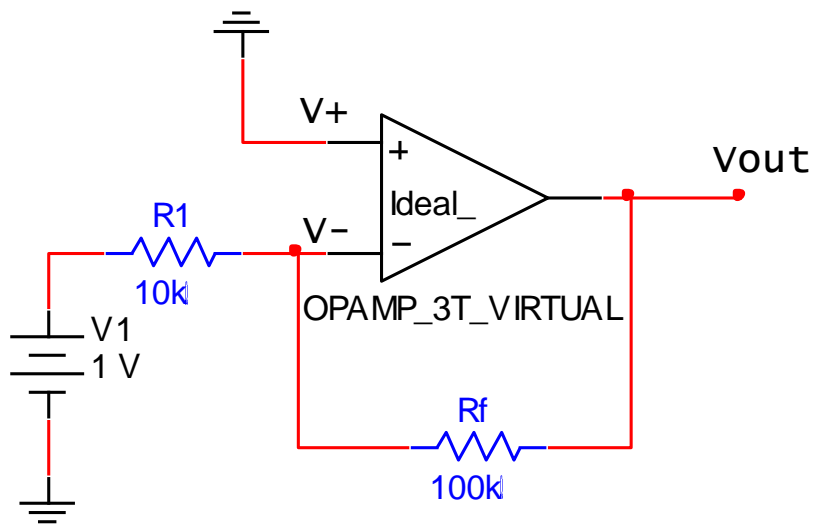


Component Level Laboratory

Analog Power Source Fundamentals (VCCS, CCVS,)

1. Inverting Op Amp Circuit:

For the circuit shown below, calculate the listed circuit parameters and the gain of the Op Amp circuit.



a. V_{R1} : _____

b. V_{Rf} : _____

c. V_+ : _____

d. V_- : _____

e. I_- : _____


f. V_{out} : _____

g. I_{Rf} : _____

h. Gain: _____

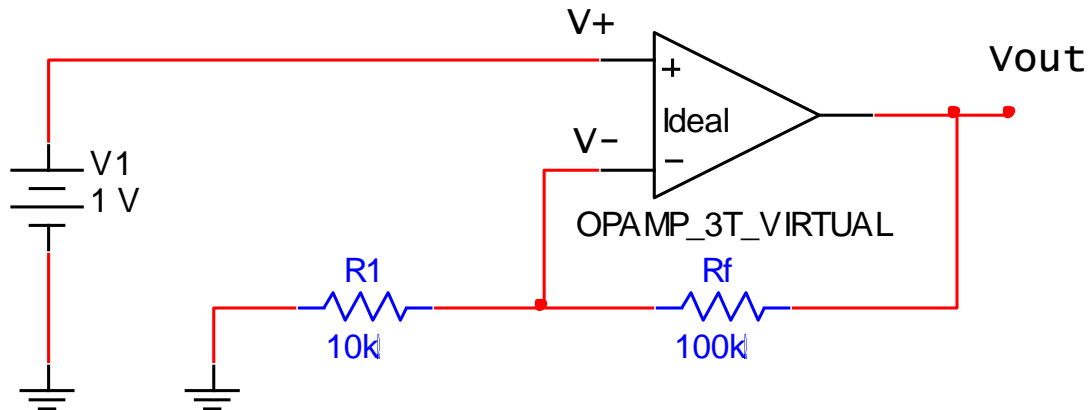2. Non-Inverting Op Amp Circuit:

For the circuit shown below, calculate the listed circuit parameters and the gain of the Op Amp circuit



a. V_{R1} : _____

b. V_{Rf} : _____

c. V_+ : _____

d. V_- : _____

e. I_+ : _____


f. V_{out} : _____

g. I_{Rf} : _____

h. Gain: _____

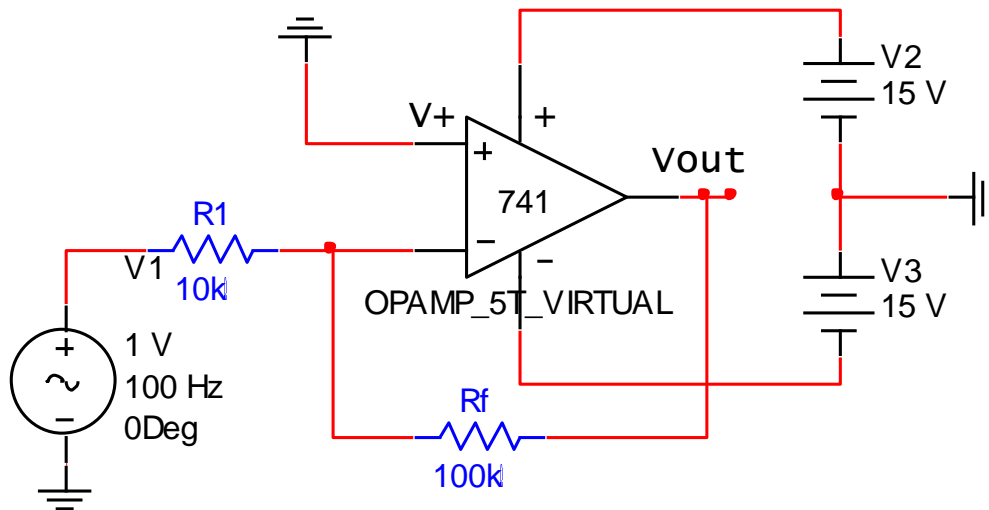3. Voltage Controlled Voltage Source (VCVS) using Non-inverting Op Amp

For a non-inverting Op Amp circuits shown below ($R_1=10K\Omega$, $R_f = 100K\Omega$), calculate the expected closed-loop voltage gain and the input impedance.



a. Close Loop Gain: _____

b. Z_{in} : _____

c. V_{out} : _____

d. V_- : _____

(1) Apply an input voltage of 1 VDC to the circuit (as shown), calculate the voltage gain from the circuit (V_{out}/V_{in}): _____

(2) Apply a sinusoidal input voltage with 1V peak ($f = 100\text{Hz}$) as input voltage, calculate the voltage gain of the circuit (V_{out_peak}/V_{in_peak}): _____; determine the phase relationship of the V_{in} and V_{out} : _____.

4. Voltage Controlled Current Source (VCIS)


For the Op Amp circuit shown below, calculate the trans-conductance, the current through R_L , the minimum and maximum resistance value of R_L for proper operation of the circuit:

a. g_m : _____

b. I_{R_L} : _____


c. $R_{L_{min}}$: _____

d. $R_{L_{max}}$: _____

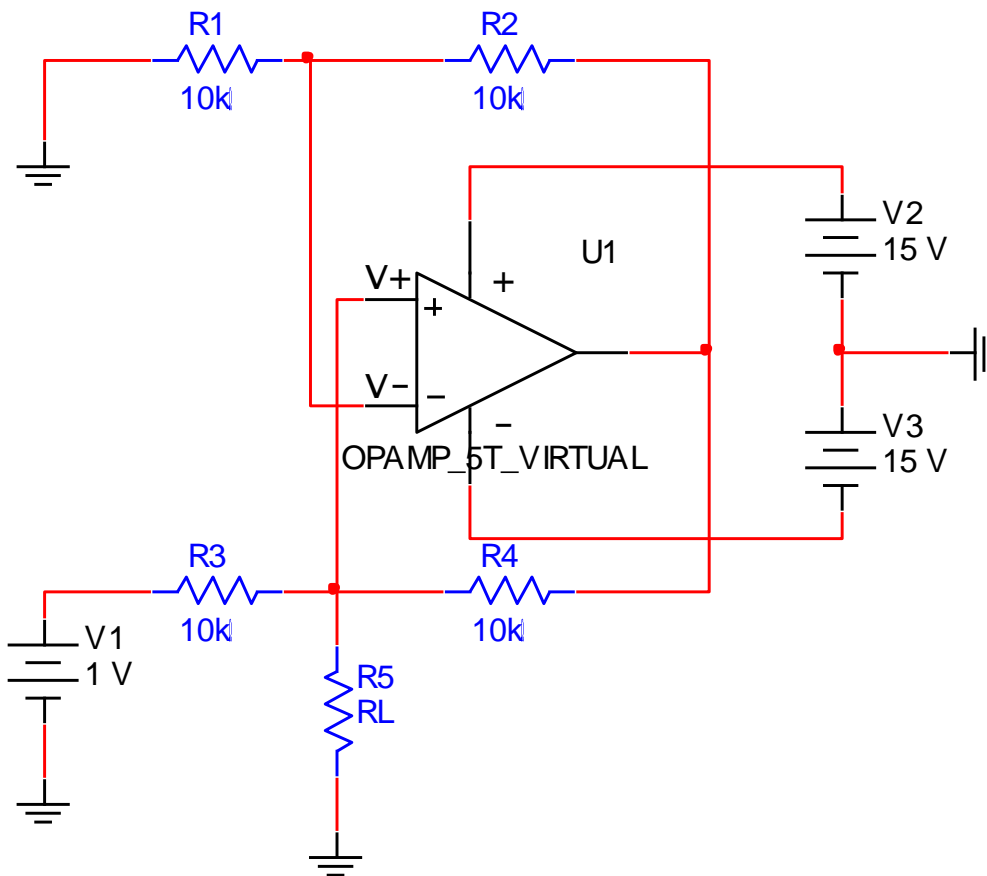

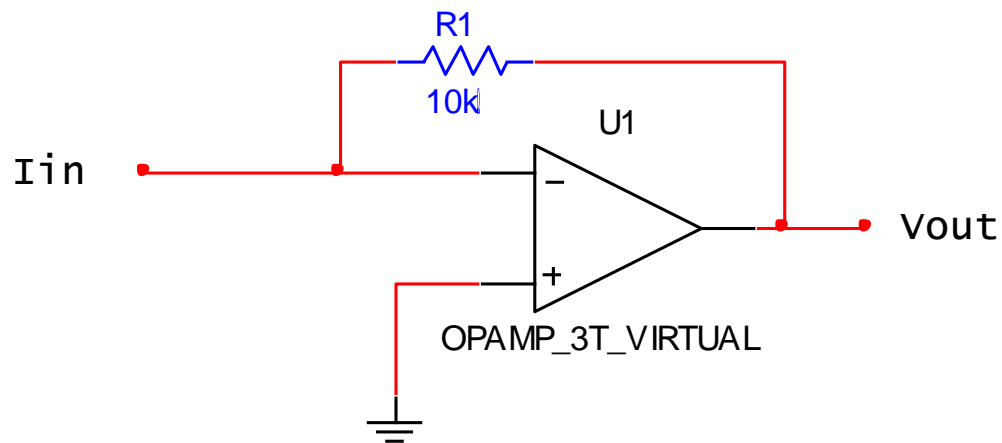5. Current Controlled Voltage Source (ICVS)

For the ICVS using Op Amp circuit shown below, calculate the trans-resistance of the circuit, the output voltage V_{out} when $I_{in} = 0.1$ mA



a. R_m : _____

b. V_{out} : _____

Reminder: Bring your breadboard to the lab!